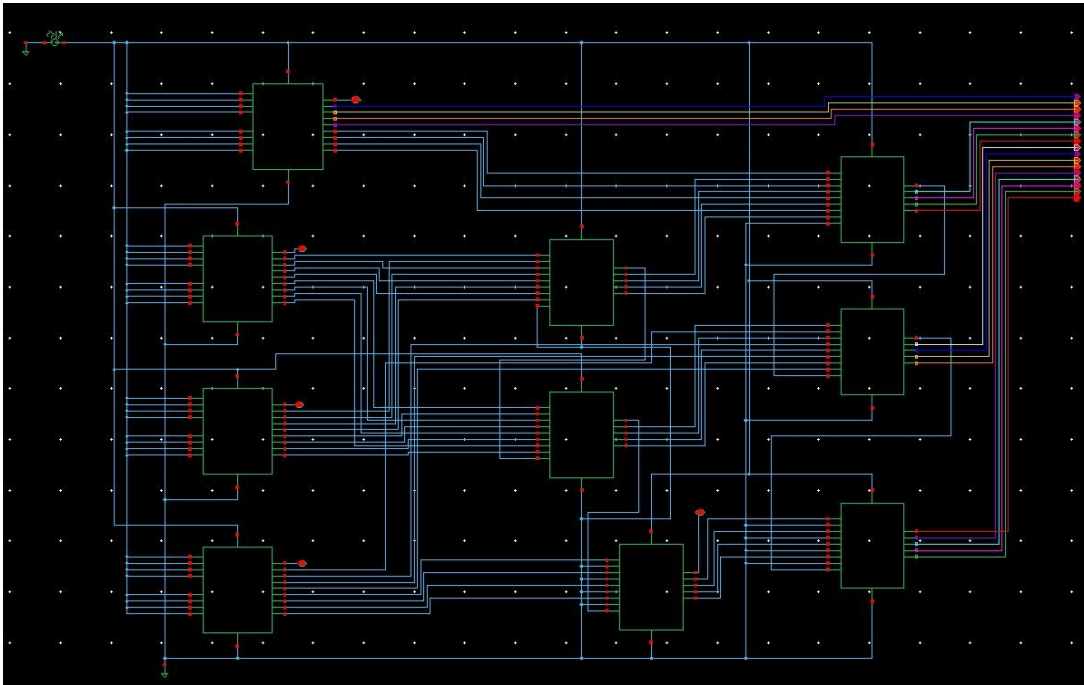


Low Power Approximate Multipliers using Compressors

- Objective: Design and implement an energy efficient multiplier using approximate compressors and encoded partial products.
- Motivation: Approximate computing reduces power and area with minimal accuracy loss.
- Block diagram of the 8x8 multiplier.



Designed by:- Deepak Kumar

Exact 4x4 Multiplier

- In the multiplication of 2 4-bit terms the product is coming in stages
- In stage 1, half adder can simply use to produce sum as (γ_1) and carry (c_1) for next stage.
- In stage 2, there are already 3 partial product terms present, so we require 4:2 compressor that takes c_1 and 3 pp terms as input and gives sum bit (γ_2) and carry (c_2) for next stage.

ORIGINAL PARTIAL PRODUCT OF THE MULTIPLICATION


Stage 7	Stage 6	Stage 5	Stage 4	Stage 3	Stage 2	Stage 1	Stage 0
	$pp_{3,3}$	$pp_{3,2}$	$pp_{3,1}$	$pp_{3,0}$	$pp_{2,0}$	$pp_{1,0}$	$pp_{0,0}$
		$pp_{2,3}$	$pp_{2,2}$	$pp_{2,1}$	$pp_{1,1}$	$pp_{0,1}$	
			$pp_{1,3}$	$pp_{1,2}$	$pp_{0,2}$		
				$pp_{0,3}$			
γ_7	γ_6	γ_5	γ_4	γ_3	γ_2	γ_1	γ_0

Theoretical Background

- Overview of Approximate 4:2 Compressor :

a . Exact 4:2 Compressor uses XOR, AND, OR that gives high power & delay.
 
$$\begin{aligned} Sum &= x_1 \oplus x_2 \oplus x_3 \oplus x_4 \oplus C_{in}, \\ C_{out} &= (x_1 \oplus x_2) \cdot x_3 + \overline{(x_1 \oplus x_2)} \cdot x_1, \\ Carry &= (x_1 \oplus x_2 \oplus x_3 \oplus x_4) \cdot C_{in} + \overline{(x_1 \oplus x_2 \oplus x_3 \oplus x_4)} \cdot x_4. \end{aligned}$$





b. Modified compressor : Ignoring XOR gates(high delay) and C_{out} (doesn't impact much on accuracy)is our goal.

By ignoring this there are 5/7 error values in carry/sum; to incorporate this error we give the inputs to compressor using propagate and generate signals.

Propagators


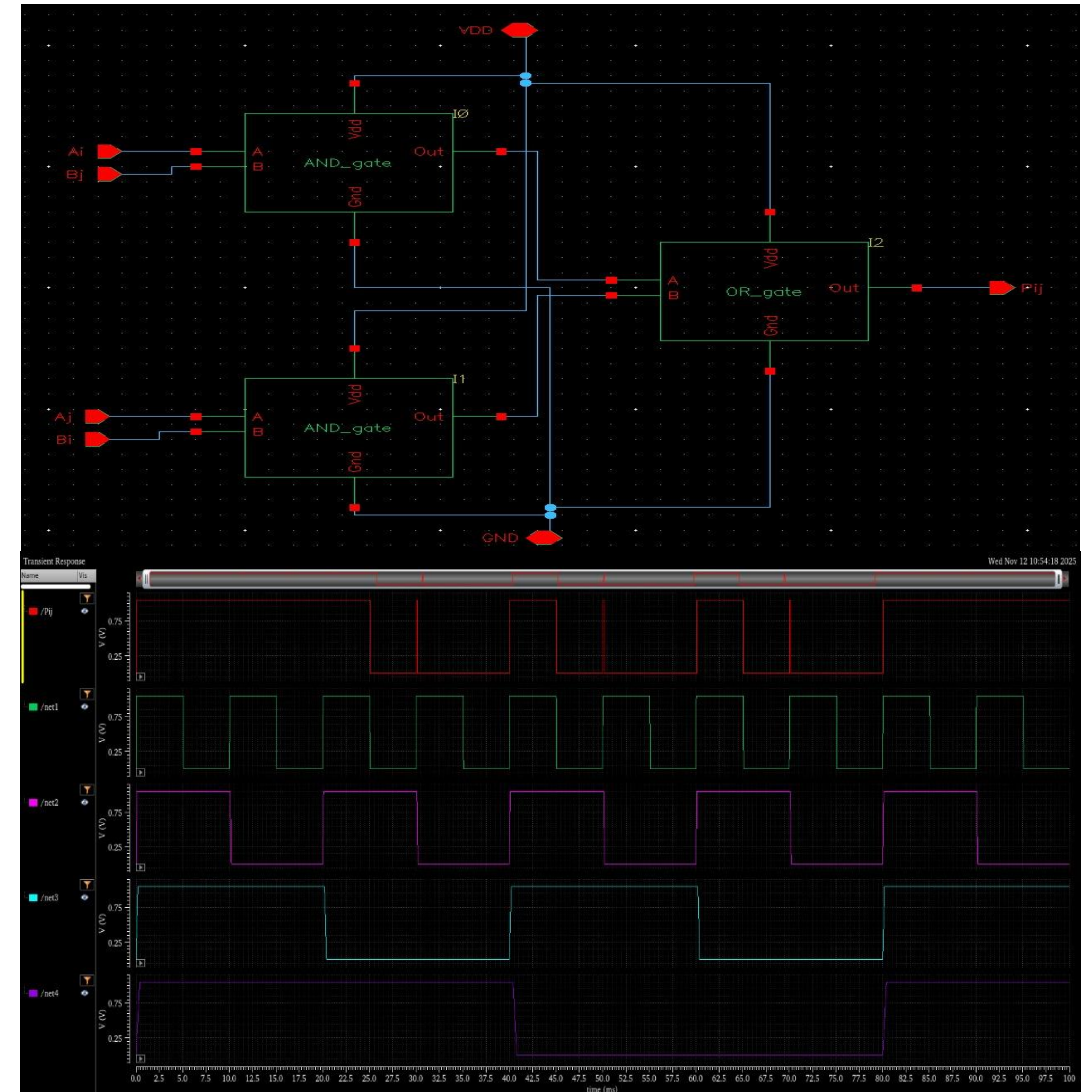
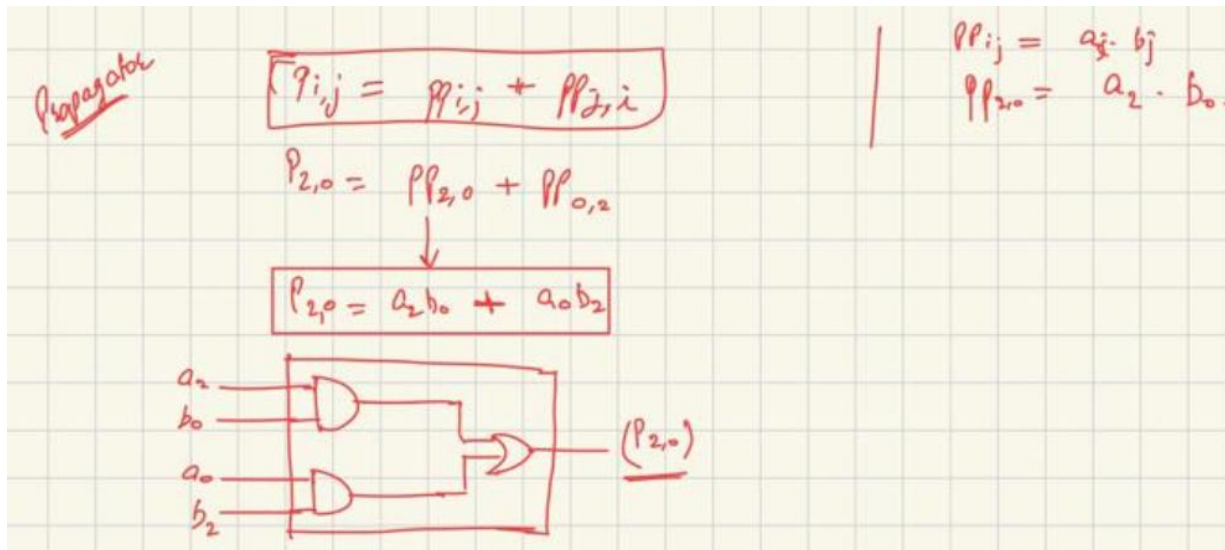
It performs logical OR of two partial products.



Designed by:- Deepak Kumar

Generators

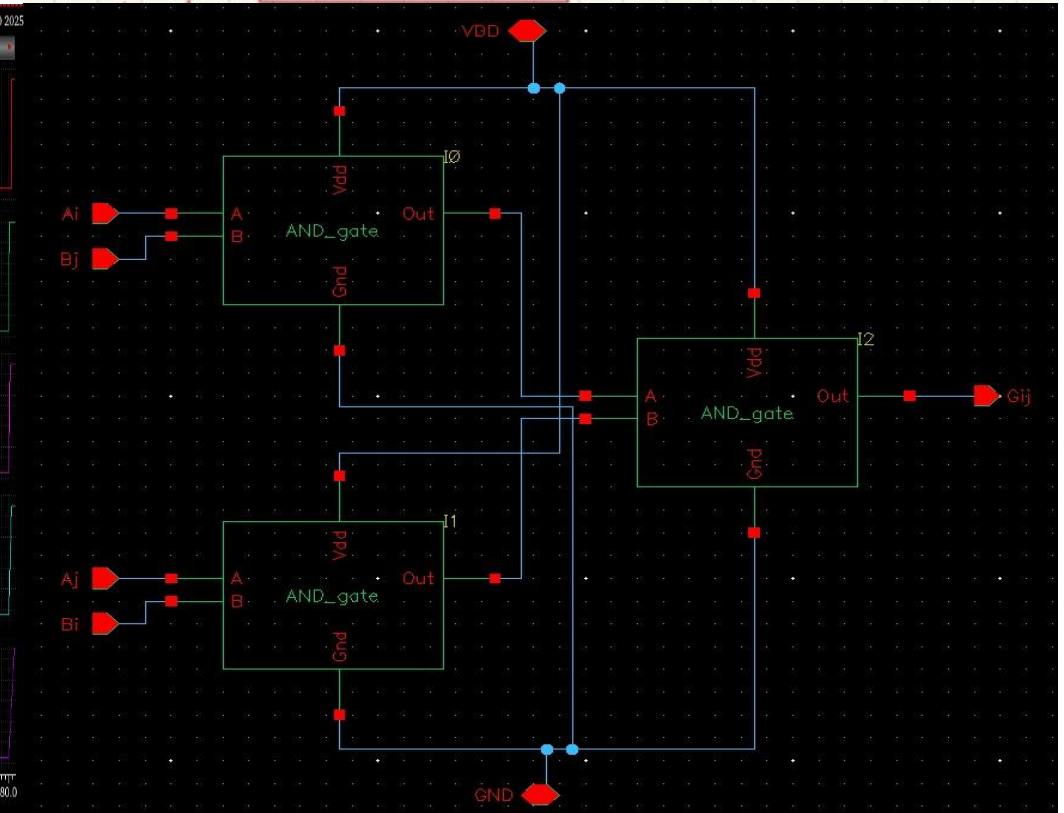  
It performs logical AND of two partial products.



Designed by:- Deepak Kumar

Stage 2 Compressor


 
- Inputs: G_{20} , P_{20} , pp_{11} and carry c_1 .
- Simplified Logic (from paper eq. 3):
- $\text{Sum} = x1 + x3$, $\text{Carry} = x2 + x4$
- Reduced from 5/7 faulty outputs to 2/4 faulty outputs.



Designed by:- Deepak Kumar

Stage 3 Compressor

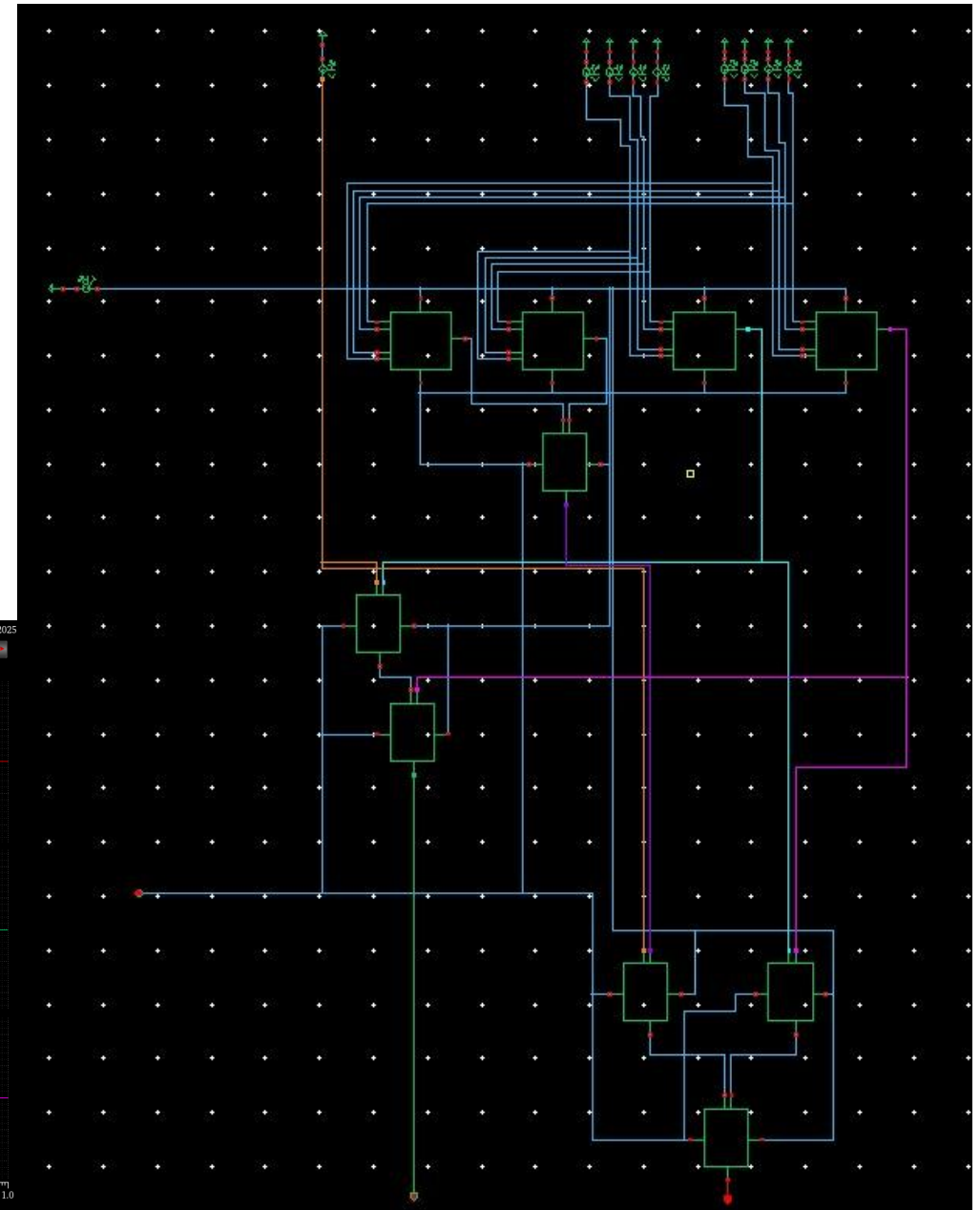
 
- Inputs: c_2 , $G_{30}+G_{21}$, P_{21} , P_{30}
- Logic Simplification (from paper Eq. 5):
- $\text{Sum} = x1+x3+x4$, $\text{Carry} = (x1.x2) + (x3.x4)$
- Acts like a 5:2 compressor with reduced complexity.



Designed by:- Deepak Kumar

Stage 4 Compressor

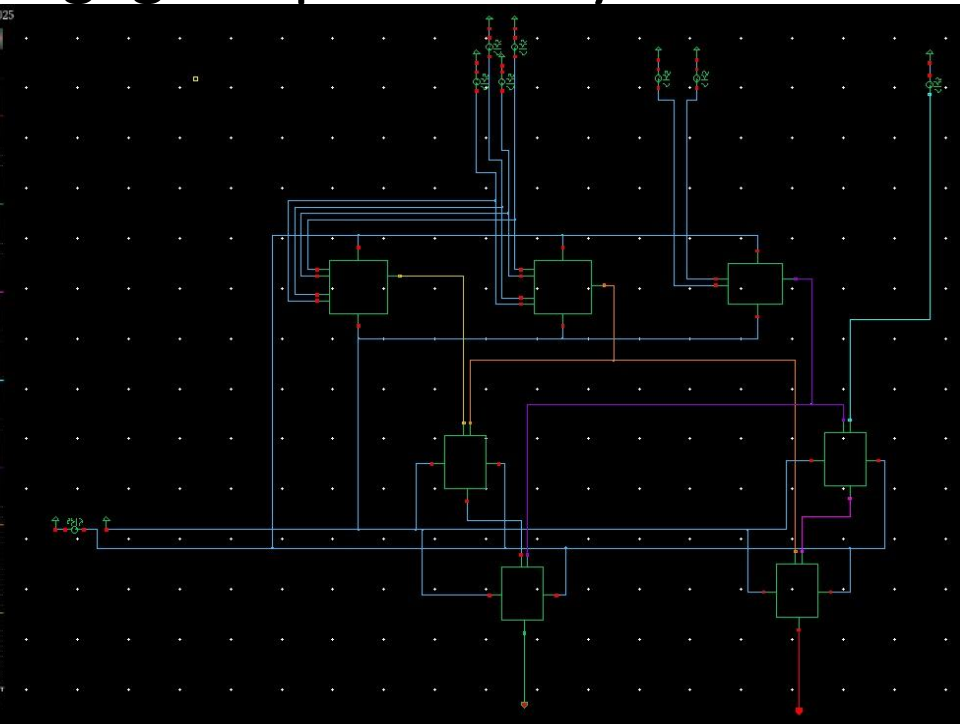
 
- Inputs: G_{31} , P_{31} , pp_{22} , and c_3 .
- Simplified logic (from paper Eq. 6):
- $\text{Sum} = x1+x2+x3$, $\text{Carry} = x2 + (x3.x4)$
- Number of error cases further reduced with negligible probability.



Designed by:- Deepak Kumar

Final Implementation of 4x4

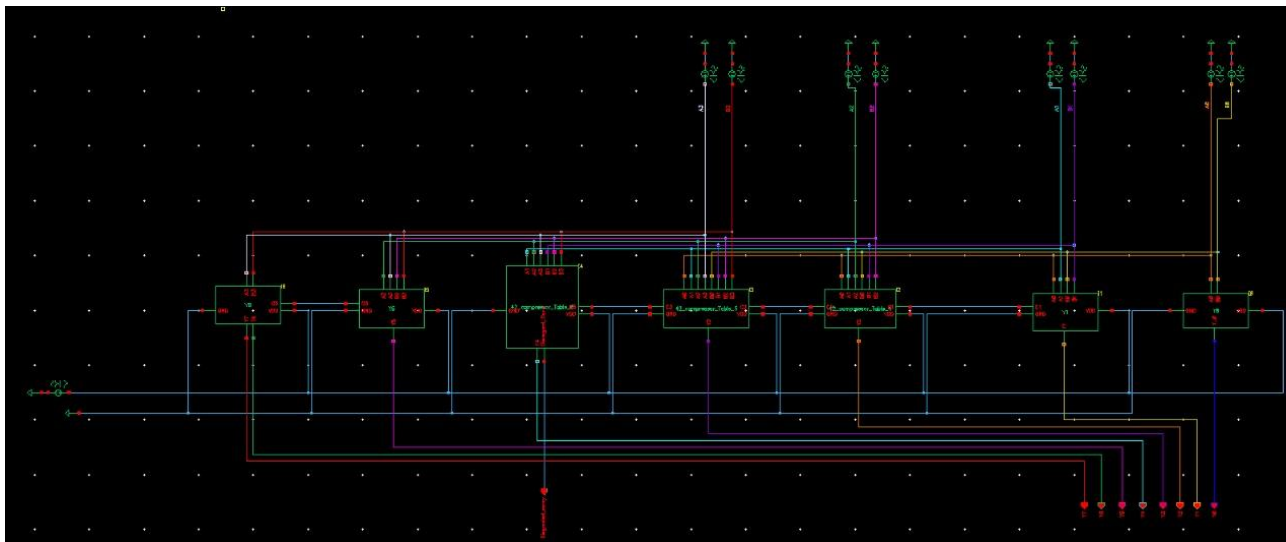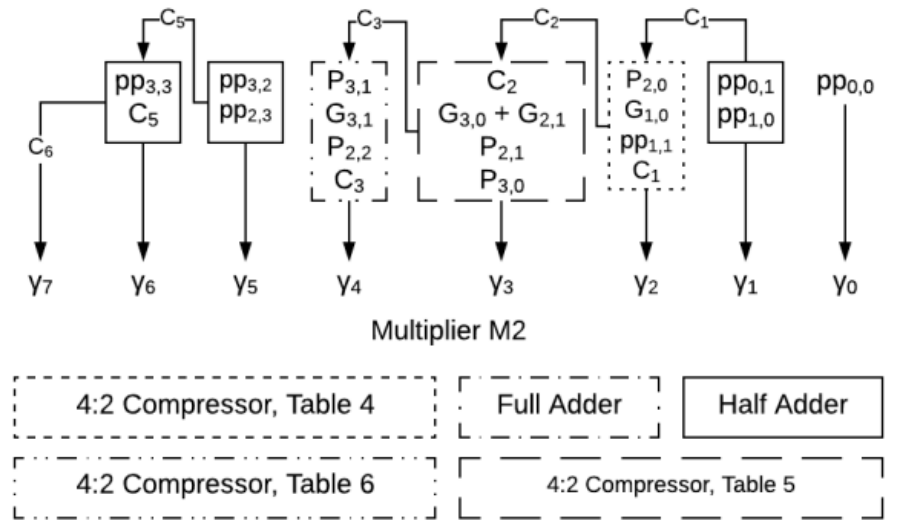- Combined the Stage 2–4 compressors and Gij/Pij generators.
- Architecture follows the paper's **M2 design** (rejecting c_4 carry).
- As speed is high in case of M2 design compared to M1 (where c_4 is fed into stage 5 and hence reducing the speed).





Designed by:- Deepak Kumar


Building 8×8 Multiplier Using 4×4 Blocks

The 8-bit operands A and B are divided into two 4-bit halves:

- $A = \{A_H, A_L\} \rightarrow$ upper 4 bits (A_H) and lower 4 bits (A_L)
- $B = \{B_H, B_L\} \rightarrow$ upper 4 bits (B_H) and lower 4 bits (B_L)
- Each combination of these halves forms **four 4×4 multipliers**:
 - $P_1 = A_H \times B_H \rightarrow$ Most significant partial product
 - $P_2 = A_L \times B_H$
 - $P_3 = A_H \times B_L$
 - $P_4 = A_L \times B_L \rightarrow$ Least significant partial product
- These four 4×4 products are then shifted and added to form the final 8×8 result:

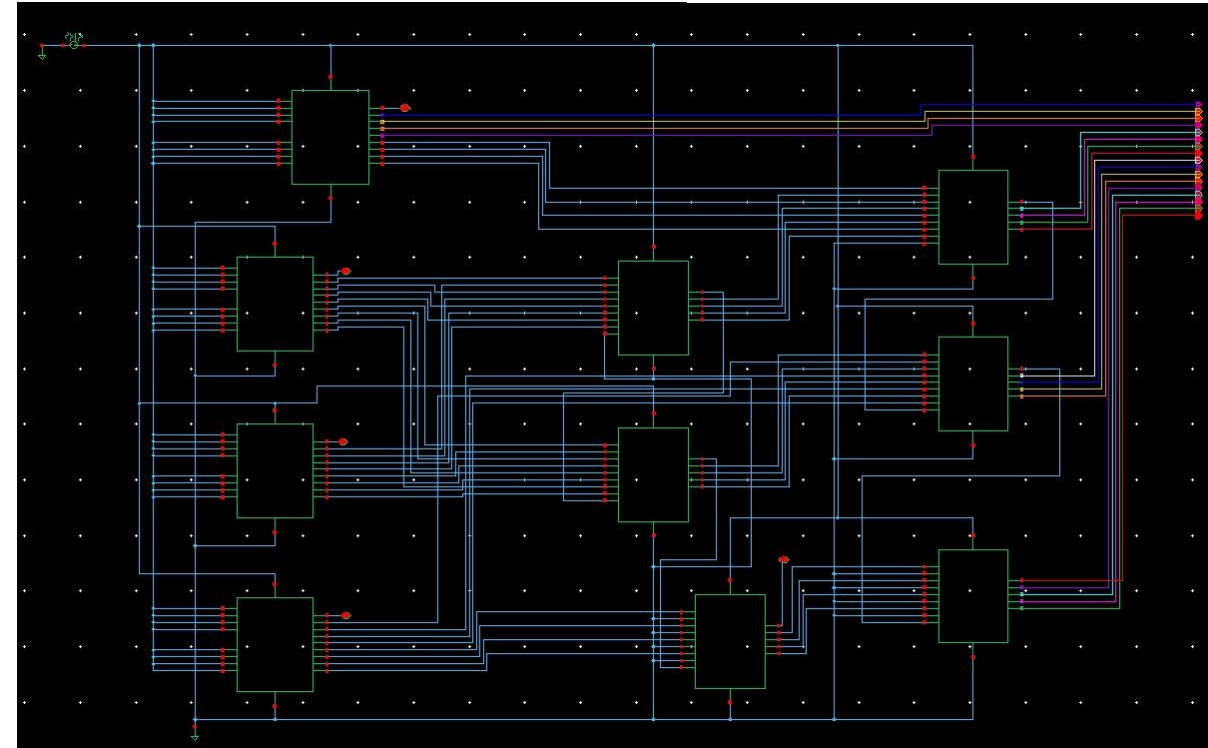
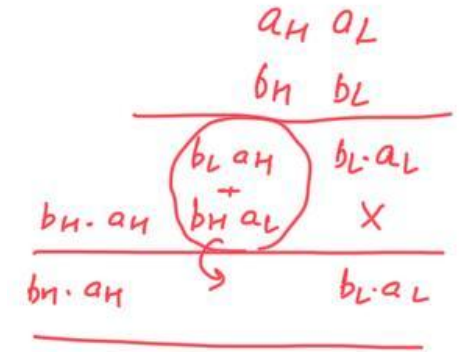


The Final Block

 

Designed by:- Deepak Kumar

Exact 8x8 Multiplier

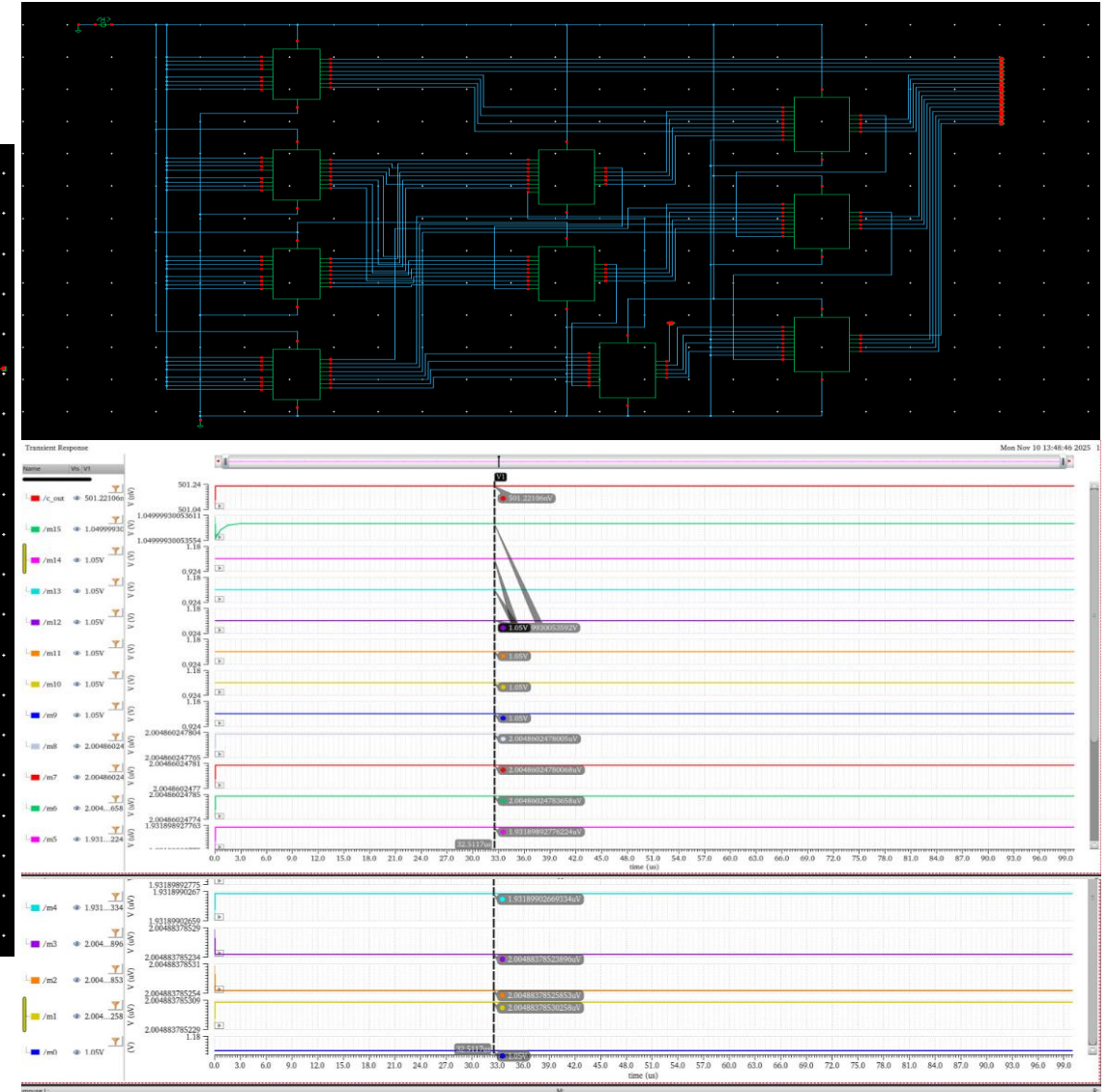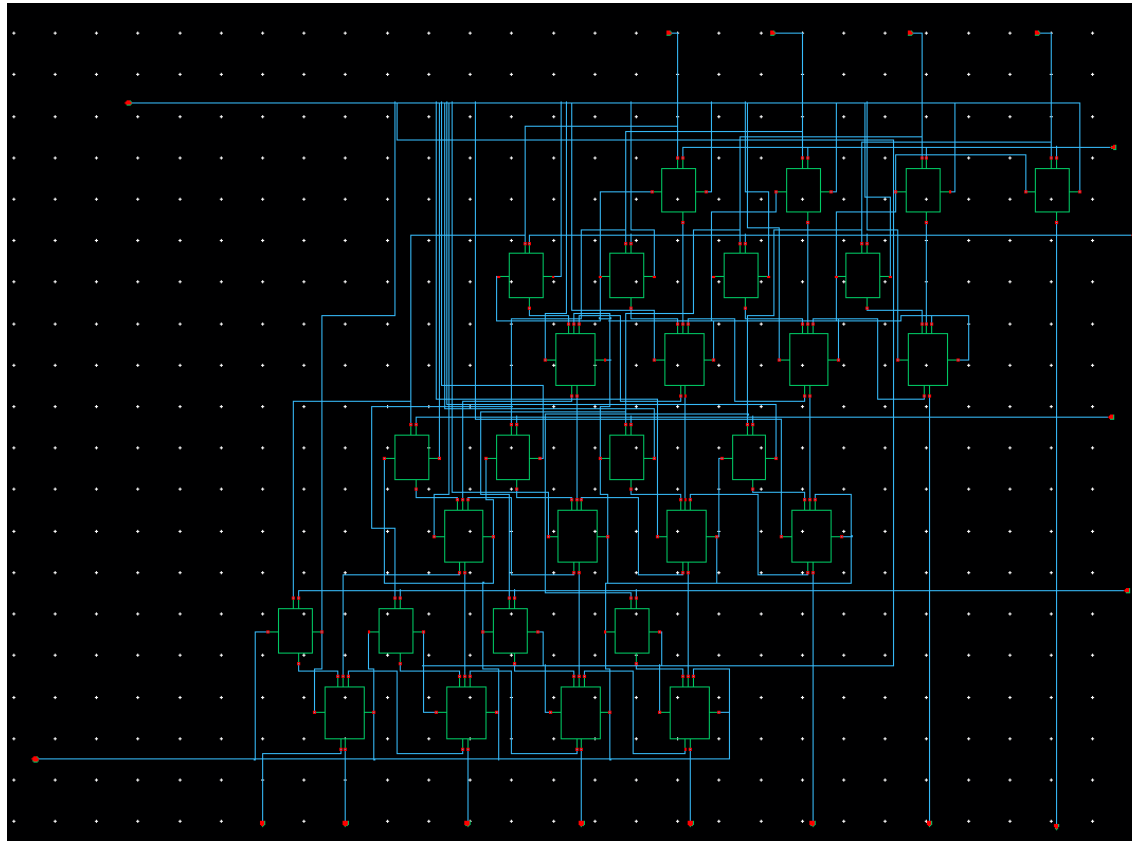

Designed by:- Deepak Kumar

Comparison Table

All the multipliers were tested with 8bit ones (255) as A and B.

Exact	Carry Disregard Approximate Multiplier	Low Power Approximate Multipliers using Compressors	Hybrid Parallel-Product High Performance Approximate Recursive Multipliers
65025	40661	45373	62241
01111111000000001	01001111011010101	01011000100111101	01111001100100001
Error Distance	6	9	4

Performance Comparison Table

We tested these multipliers for many different inputs and took average power and delay of them..

8x8 Multiplier	Average Delay	Average Power
Exact Multiplier	5.9986775 ns	477.63918 μ W
Carry Disregard Approximate Multiplier	5.7585925 ns	232.48725 μ W
Low Power Approximate Multipliers using Compressors	5.802965 ns	228.0562 μ W
Hybrid Parallel-Product High Performance Approximate Recursive Multipliers	5.916225 ns	289.4195 μ W